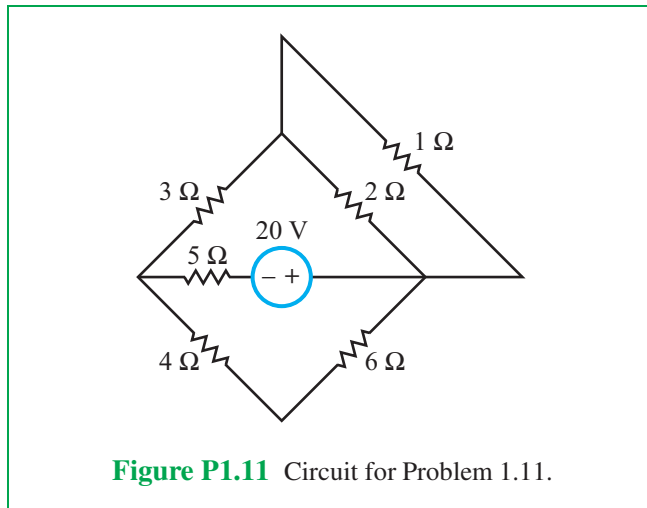


Problem 1.11 For the circuit in Fig. P1.11:

Hint: See the textbook and/or lecture notes for the difference between nodes and extraordinary nodes

- (a) Identify and label all distinct nodes.
- (b) Which of those nodes are extraordinary nodes?
- (c) Identify all combinations of 2 or more circuit elements that are connected in series.
- (d) Identify pairs of circuit elements that are connected in parallel.



Problem 1.23 The plot in Fig. P1.23 displays the cumulative amount of charge $q(t)$ that has exited a certain device up to time t . What is the current at:

- (a) $t = 2$ s
- (b) $t = 6$ s
- (c) $t = 12$ s


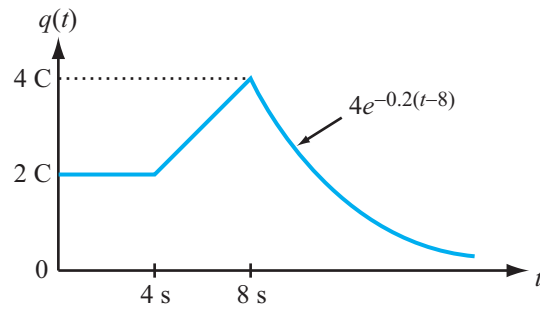


Figure P1.23: $q(t)$ for Problem 1.23.

Problem 1.25 In the circuit of Fig. P1.25, node V_1 was selected as the ground node.

- (a) What is the voltage at node V_2 ?
- (b) What is the voltage difference $V_{32} = V_3 - V_2$?
- (c) What are the voltages at nodes 1, 3, 4, and 5 if node 2 is selected as the ground node instead of node 1?

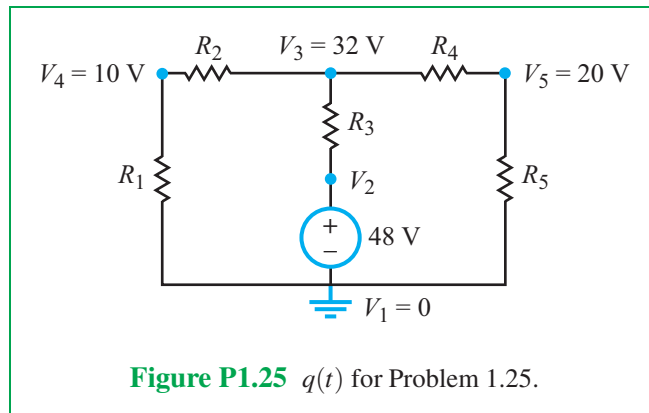

Problem 1.27 For each of the eight devices in the circuit of Fig. P1.27, determine whether the device is a supplier or a recipient of power and how much power it is supplying or receiving.


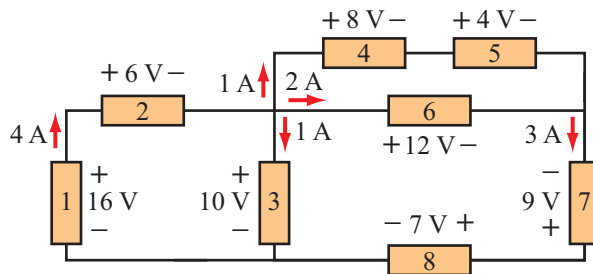


Figure P1.27: Circuit for Problem 1.27.

Problem 1.38 Determine V_y in the circuit of Fig. P1.38.

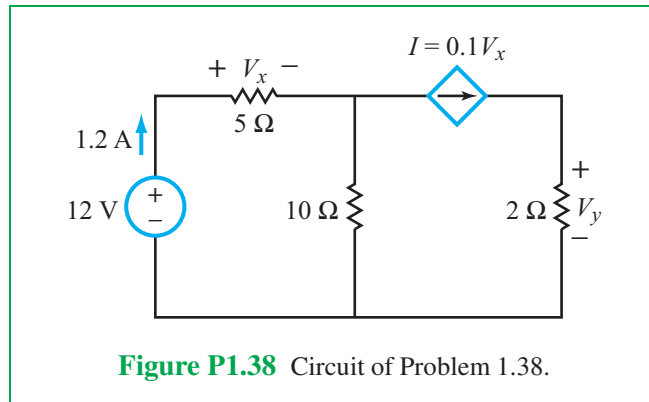

Problem 1.39 Determine V , the voltage of the dependent voltage source in the circuit of Fig. P1.39.

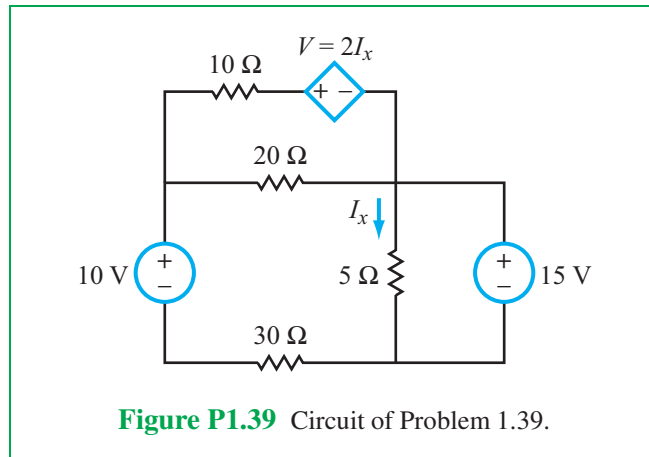


Figure P1.39 Circuit of Problem 1.39.

Problem 2.17 Determine currents I_1 to I_4 in the circuit of Fig. P2.17.

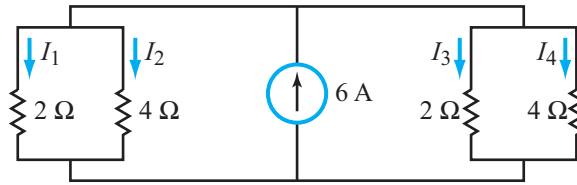


Figure P2.17: Circuit for Problem 2.17.

Problem 2.18 Determine the amount of power dissipated in the $3\text{-k}\Omega$ resistor in the circuit of Fig. P2.18.

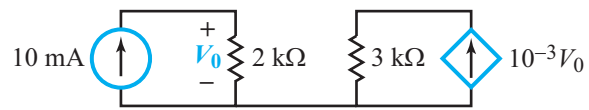


Figure P2.42: Circuit for Problem 2.18.

Problem 2.23 Determine the amount of power supplied by the independent current source in the circuit of Fig. P2.23.

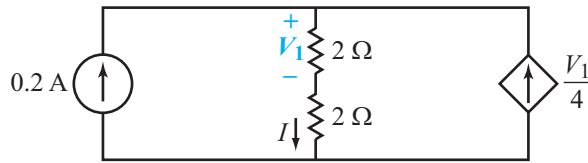


Figure P2.23: Circuit for Problem 2.23.

Problem 2.15 Determine I_x in the circuit of Fig. P2.15.

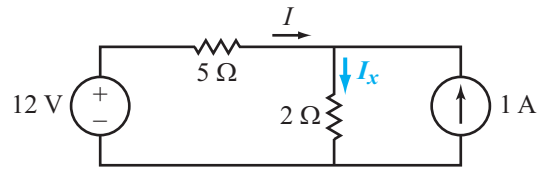


Figure P2.15: Circuit for Problem 2.15.