

**Problem 2.31** Find  $I_0$  in the circuit of Fig. P2.31. **Hint:** Use the current division method.

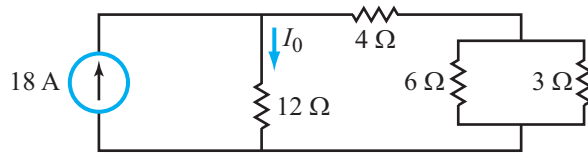


Figure P2.31: Circuit for Problem 2.31.

**Problem 2.33** Determine  $R_{eq}$  at terminals  $(a, b)$  in the circuit of Fig. P2.33.


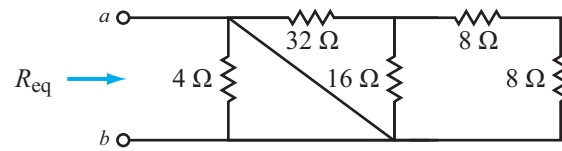


Figure P2.33: Circuit for Problem 2.33.


**Problem 2.39** Find  $R_{\text{eq}}$  at terminals  $(c, d)$  in the circuit of Fig. P2.38.

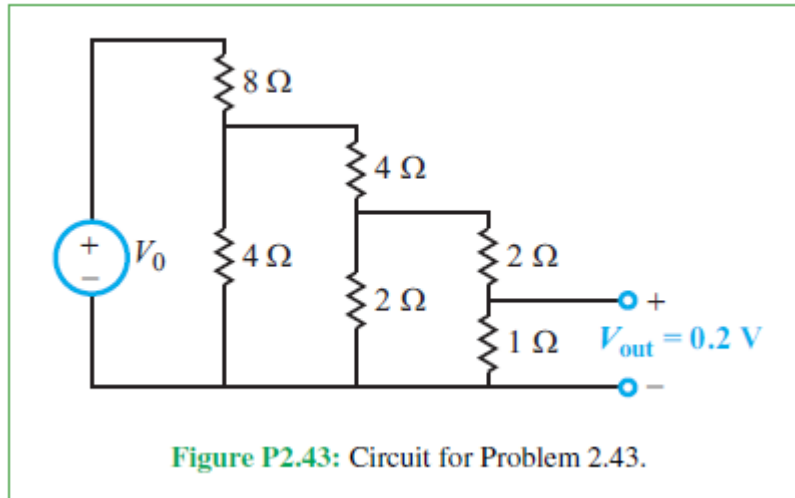


**Problem 2.43** Apply voltage and current division to determine  $V_0$  in the circuit of Fig. P2.43 given that  $V_{\text{out}} = 0.2 \text{ V}$ .



**Problem 3.20** For the circuit in Fig. P3.20, determine the current  $I_x$ . Use Node-Voltage Technique.

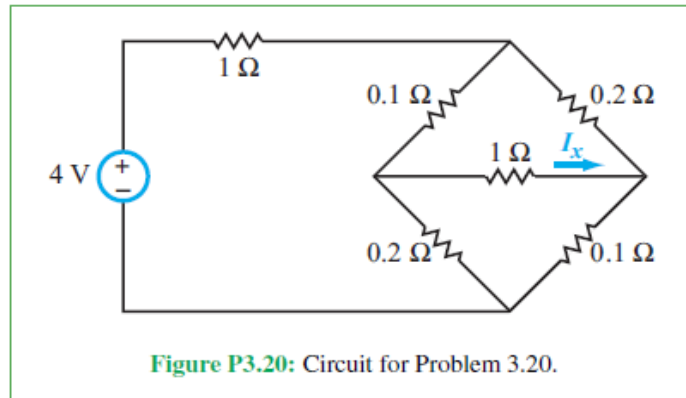


**Problem 3.15** Use the supernode concept to find the current  $I_x$  in the circuit of Fig. P3.15.

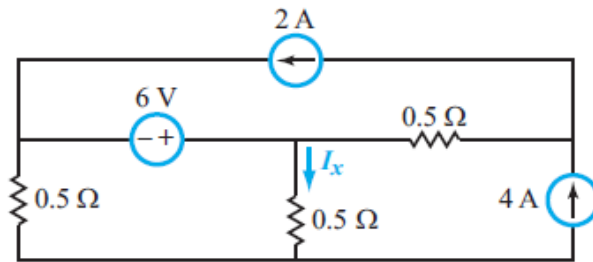

**Figure P3.15:** Circuit for Problem 3.15.

**Problem 3.17** Determine  $V_x$  in the circuit of Fig. P3.17. Use Node-Voltage Technique.

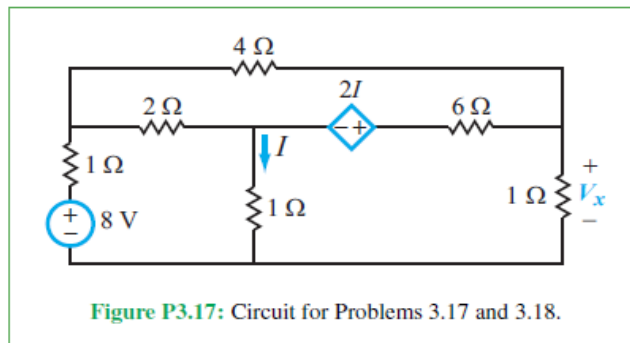

**Problem 3.43** Apply mesh analysis to the circuit of Fig. P3.43 to find  $I_x$ .


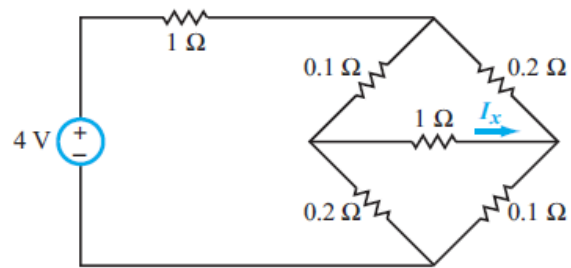


Figure P3.43: Circuit for Problem 3.43.

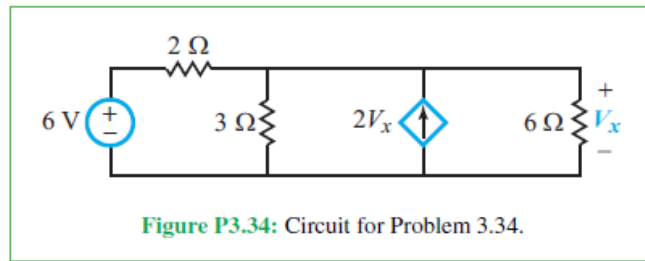

**Problem 3.34** Apply mesh analysis to the circuit in Fig. P3.34 to determine  $V_x$ .



**Problem 3.47** Apply mesh analysis to determine  $I_0$  in the circuit in Fig. P3.47.

